

# More About the Three-Control Six-Band 813 Transmitter

*Supplementary Data on the 500-Watt Rig*

BY C. VERNON CHAMBERS,\* W1JEQ

**M**OST of those who have had previous experience in building a multistage transmitter have had little difficulty in duplicating the 813 rig described in *QST* for January, 1954.<sup>1</sup> However, many who have made this their first major attempt at construction have run into various stumbling blocks or have been uncertain about specific points. There are others who have asked about such things as a simple method of installing a differential keying system and a suitable antenna tuner. We will try to cover the points brought up most frequently.

Some of those who have written in more recently have apparently overlooked the second article which dealt with some of the problems. If you missed it, look in *QST* for June, 1955.<sup>2</sup>

\* Technical Assistant, *QST*.

<sup>1</sup> Chambers, "Three-Control Six-Band 813 Transmitter," *QST*, January, 1954. Also *The Radio Amateur's Handbook*, 31st-33rd editions.


<sup>2</sup> Chambers, "Supplementary Data on the Three-Control 813 Transmitter," *QST*, June, 1954.

• The 813 transmitter described originally in *QST* for January, 1954, and carried in subsequent editions of the *ARRL Handbook*, still continues to enjoy widespread popularity. Answering several hundred inquiries during the past 2½ years has given us an opportunity to find out the things that most often bother the ham in duplicating the performance of the original. This article covers these problems and also the matters of coupling to an antenna system and the installation of a differential keying system.

## Drive to the 813

The most common difficulty reported is inadequate drive for the final at the higher frequencies, especially 28 Mc. Fear that the driver is incap-

*Fig. 1*— This front view of the 813 transmitter identifies the decal markings for the meters and the tuning controls. Dials for the amplifier plate capacitor and the excitation control are National types AM-3 and P, respectively. The latter is no longer manufactured. The grid, plate, v.f.o. and antenna-coupler capacitors located at the bottom of the panel are equipped with National type HRS-5 (black) knobs. Type HRS-4 knobs are used with the three rotary switches.

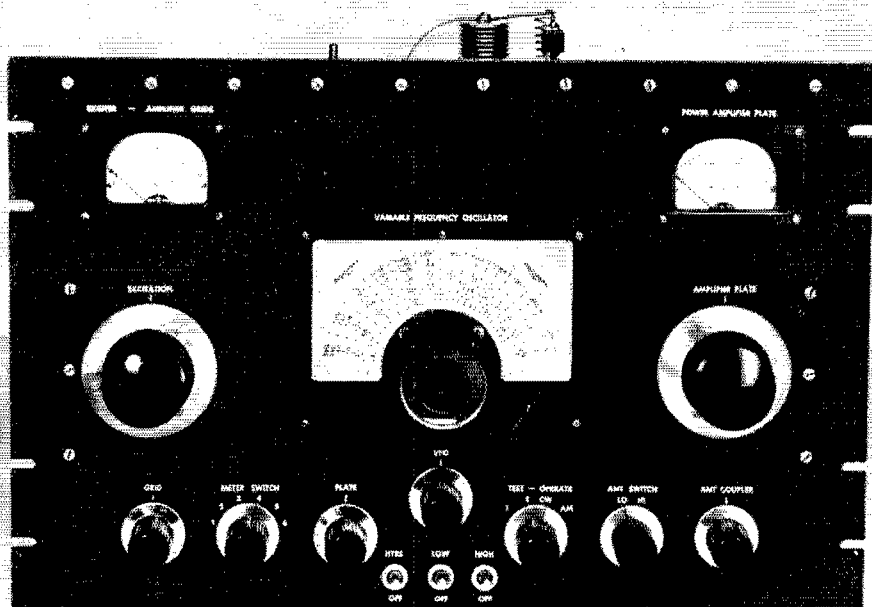



adjustment of multiband tanks has been covered in previous articles.<sup>3</sup>

### Output Impedance, Antenna Couplers and Antennas

These three subjects are grouped under a common heading because of their close relationship. And let's start out by clearing up the fairly prevalent opinion that there is something tricky about the output-coupling circuit ( $L_8C_{10}S_2$ ). Except for a simple-switching arrangement which shorts out the unused part of the link winding, it is identical to the series-tuned arrangement commonly used for coupling amplifiers to 50-ohm coaxial lines. Anyone interested in the circuit will find the required reading under "Output Coupling Systems" in Chapter 6 of *The Radio Amateur's Handbook*.

Several constructors who encountered difficulty loading the 813 transmitter discovered that they had improperly wired the  $C_{10}L_8S_2$  combination. To prevent others from making the same mistake, we offer the following:

A tap on  $L_8$  — the one that goes to  $C_{10}$  and  $S_{2B}$  — effectively divides the inductor into two sections. The 8-turn section is used for coupling to the LO-BAND plate inductor,  $L_7$ , and the 1-turn link is used for coupling to  $L_9$  at 14 through 28 Mc. There are two precautions to observe when installing this tapped coil. First, make certain that the small link is adjacent to  $L_9$ . This, in

<sup>3</sup> Johnson, "Multiband Tuning Circuits," *QST*, July, 1954.

Chambers, "Single-Ended Multiband Tuners," *QST*, July, 1954.

turn, will place the 8-turn section next to  $L_7$ . Second, carefully study the transmitter diagram before wiring  $L_8$  to  $S_2$ . It is very easy to end up with the wrong link shorted when the switch is thrown to either the LO- or HI-BAND positions. The circuit of the transmitter shows the switch in the 3.5-7-Mc. position.

The transmitter output circuit is designed to feed a 50-ohm resistive load. This doesn't mean feeding a 50-ohm coax line with any old antenna connected at the other end. Unless the antenna is matched to the line, it will introduce reactance in the output coupling circuit and cause the amplifier plate capacitor,  $C_9$ , and the output capacitor,  $C_{10}$ , to resonate at dial settings that do not coincide with those previously listed.<sup>1</sup> To operators having no prior working acquaintance with coaxial output systems, we recommend "Matching the Load to the Line," Chapter 13, *The Radio Amateur's Handbook*, as a complete source of information on any adjustments which may be necessary to match the antenna to the transmission line.

If the antenna to be used with the transmitter is fed with an open-wire line or is a high-input-impedance affair, it is advisable to use a coax-coupled matching circuit between the transmitter output and the antenna or feedline. The 500-watt antenna coupler described in the "Coupler or Matching-Circuit Construction" section of Chapter 13 (*Handbook*) is ideal for coupling most of the popular all-band antennas to the 813 rig. Another section of Chapter 13, "Coupling the Transmitter to the Line," explains how the an-

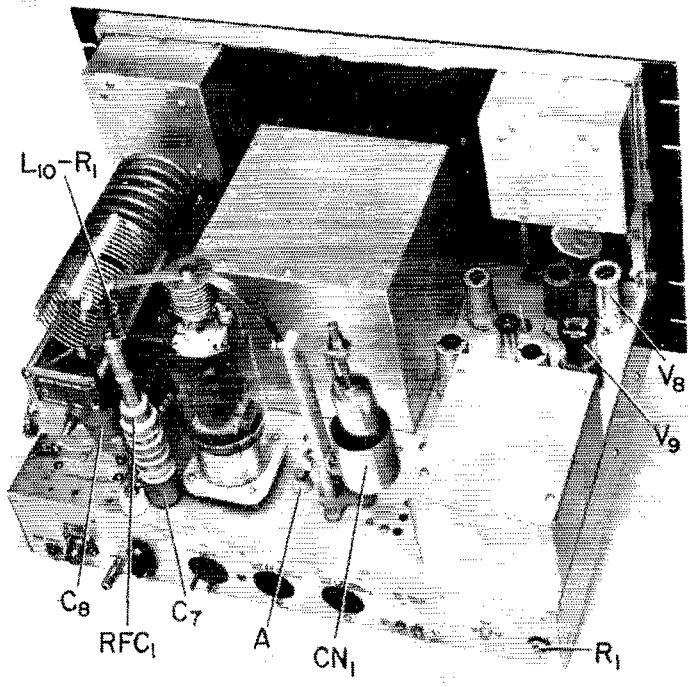


Fig. 3 — Rear view of the modified 813 transmitter. The type R-175A choke is mounted on  $C_7$  (original component) to the left of the tube. The parasitic trap,  $L_{10}R_1$ , is at the top of the choke and the neutralizing capacitor,  $CN_1$ , is to the right of the 813. Keyer tubes are to the right of the buffer and the multiplier tubes in the upper right-hand corner of the chassis.

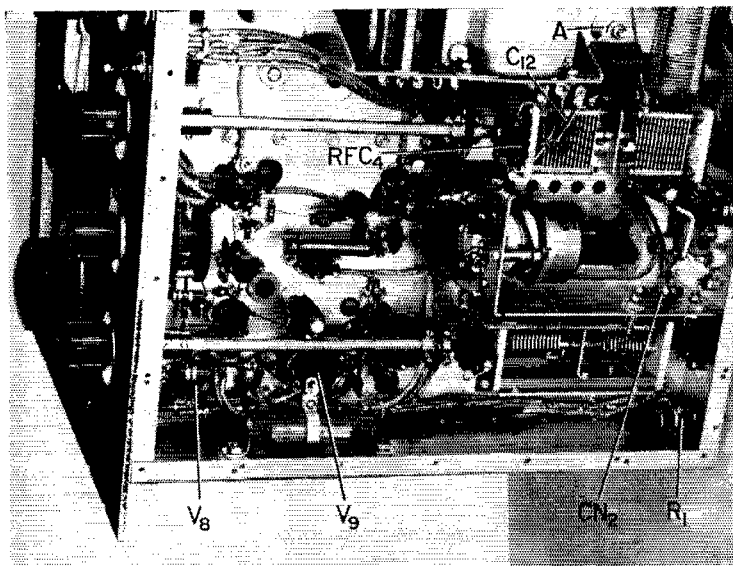


Fig. 4— In this view, the potentiometer for the keyer control-tube,  $V_{8A}$ , is mounted on the wall at the bottom right-hand corner of the chassis as seen in this view. The neutralizing capacitor for the 6146,  $C_{N2}$ , is supported by National TPB through-point bushings. Sockets for the keyer tubes are in the lower left-hand section of the unit and the 20-watt adjustable resistor is mounted on the bottom wall.

tenna-coupler adjustments may be speeded up and checked with the aid of an s.w.r. bridge.

#### Neutralization, Parasitics, and R.F. Feed-Through

The second article on the 813 transmitter<sup>2</sup> explained why some duplicates of the rig might require neutralization and suggested the *Handbook* capacitive-bridge system as a cure for instability. This bit of information has prompted a number of inquiries. Some reported the need for neutralization and questioned the effectiveness of the recommended neutralizing circuit. Others asked if a neutralizing circuit would clean up certain erratic current readings observed while tuning the final. And still others referred to r.f. feed-through (from grid to plate of the amplifier when operated without plate and screen voltage) detected by one means or another.

The first step toward the cure for instability is the grounding of the beam-forming plates (Pin 5) of the 813 as recommended earlier.<sup>2</sup> Following the usual practice at that time, the transmitter diagram did not show this connection.

If instability is encountered in a rig having Pin 5 grounded, attempt to determine the frequency of oscillation. Three common types of oscillation may take place in an amplifier. Since different measures must be taken to suppress each type, it is important that the type be identified before it can be treated intelligently. V.h.f. and low-frequency parasitic oscillations are difficulties that may or may not pop up in a duplicate transmitter and either one can cause erratic meter readings. The methods of testing, and the remedies for these types of oscillation are thoroughly treated in "Stabilizing Amplifiers," Chapter 6 of the *Handbook*.

Should the oscillation be at the fundamental frequency, it may quit when a load is coupled to the amplifier. When loading fails to stabilize

the output stage, check the performance of each exciter tube—one of them may be oscillating hard enough to drive the final during key-up periods. The *Handbook* section referred to above explains how the tests should be made.

When the need for neutralization has become an established fact, consider use of the capacitive-bridge system previously referred to.<sup>2</sup> Fig. 2 shows this circuit applied to the original 813 amplifier. As far as neutralization is concerned,  $C_{N1}$  is the only addition to the amplifier. However, it was necessary to reduce the value of  $C_{12}$  (originally 0.001  $\mu\text{f.}$  and not labeled) to 390  $\mu\text{f.}$  to make the ratio of  $C_{N1}$  to  $C_{12}$  equal the ratio of the tube grid-plate capacitance to the input capacitance (see *Handbook*). The value of  $RFC_4$  (not labeled on the transmitter circuit diagram) has been increased to 2.5 mh., and  $L_{10}$  and  $R_1$  have been added to suppress low-frequency and v.h.f. parasitics that developed after the amplifier had been modified for neutralization, and the National type R-175A plate choke had been substituted. More about the choke later on.

The neutralizing capacitor is mounted on the chassis as shown in Fig. 3. A feed-through bushing, A, to the left of  $C_{N1}$  permits connection between the stator side of the capacitor and the grid circuit. Strips of  $\frac{3}{8}$ -inch-wide flashing copper are used for above-chassis leads to the capacitor. A heat-radiating plate cap for the 813 serves its intended purpose and also provides a convenient means of terminating the copper leads running to  $C_{N1}$  and the parasitic trap. Fig. 4 shows the positions of the feed-through bushing, A,  $C_{12}$  and  $RFC_4$  as viewed from the bottom.

Neutralizing adjustments are also described in Chapter 6 of the *Handbook*. The section about this subject should also be reviewed for information about r.f. feed-through (mentioned earlier). Note in particular that feed-through cannot always be reduced to zero but that the correct

adjustment should give a *minimum* reading on the r.f. indicator. The sensitivity of the indicator will frequently determine whether or not the reading can be reduced to zero.

The 6146, when operated straight through, is probably the only driver tube that may require neutralization. We were able to *make* the stage oscillate weakly and intermittently, but only after increasing plate and screen voltage, removing excitation and adjusting the grid and plate controls to settings not normally used. All of this was done so that the capacitive neutralizing system could be tried in this stage. The system did work and required neutralizing and grid bypass capacitances of approximately 1.5 and 500  $\mu\text{mf.}$ , respectively. This means that the 0.001- $\mu\text{mf.}$  capacitor formerly used between  $C_4$  and ground must be replaced with the 500- $\mu\text{mf.}$  unit. The neutralizing capacitor, labeled in Fig. 4 as  $CN_2$ , may be a pair of 3- $\mu\text{mf.}$  ceramic tubulars connected in series. Incidentally, several makes of TV-type tubular trimmers broke down when tried in the neutralizing circuit.

A low-frequency parasitic that turned up in the multiplier-driver stage after neutralizing components had been installed was killed by replacing the 1-mh. grid choke with a 2.5-mh. job. This oscillation occurred only when the plate voltage for  $V_5$  was increased to 450 volts or above.

### Keying

Although the 813 transmitter employs straight cathode keying of the oscillator, we have received very few unfavorable reports concerning chirp, clicks, etc. However, many perfectionists have requested dope on a differential keyer circuit that could be added to the rig. A few hours of lab work proved that the system described by Puckett<sup>4</sup> could be easily included as an integral part of the rig. All that is required in the way of operating voltage for the keyer will be found right there in the r.f. unit.

The keying circuit uses a type 12AU7 control tube and a type 6BL7GT vacuum-tube keyer, as shown in Fig. 5. This circuit also shows the modifications which have been made to the transmitter so that the keyer could be included. The bottom end of the 47K oscillator grid resistor has been lifted from ground and then returned to Pin 1 of  $V_8$ . The original key jack,  $J_1$ , has been moved over to Pin 7 of  $V_8$ , and the bottom end of the oscillator cathode choke is now grounded. Cathode bias for the multiplier stage, previously developed across a 220-ohm resistor, has been eliminated and the cathode of  $V_5$  is returned to the plates of the 6BL7GT.

Undoubtedly, some individuals will question the advisability of keying the multiplier stage in preference to keying the following multiplier-driver. Actually, we would have preferred to key the 6146, but we felt that the voltage drop caused by the 6BL7GT (the

tube may be regarded as a cathode resistor of about 1000 ohms) would adversely affect the output capability of the tube.

Installation of the keyer components is illustrated in Figs. 3 and 4. Heater voltage for  $V_8$  and  $V_9$  may be obtained by tapping onto the heater line for the r.f. tubes. Negative control voltage for the keyer tubes may be taken from the 6146 bias supply by connecting in at the junction of the 1.2K and 10K resistors. Plate voltage for  $V_{8B}$  can come from the 300-volt line for  $V_1 - V_5$ .

Adjustment of the keying circuit and the keying characteristics are explained in Puckett's article. The only other comment about keying that we have to offer concerns bias for the final amplifier. The "beyond cut-off" bias for the original rig tended to introduce clicks *after* the keyed stage and, as a result, the fixed bias for the 813 was reduced to approximately -65 volts. This was accomplished by substituting a 4700-ohm, 2-watt resistor for the 470-ohm filter resistor used in the bias pack.

### General Information — Electrical

Yes, a National type R-175A r.f. choke may be used as  $RFC_1$  in the 813 plate circuit. However, use of this choke as a replacement for the original homemade affair did affect the tuning range of the plate tank and made necessary the removal of 1 turn from  $L_7$ . The turn was removed from the  $C_3$  end of the coil. Fig. 3 shows the R-175A mounted on  $C_7$  at the rear of the chassis.

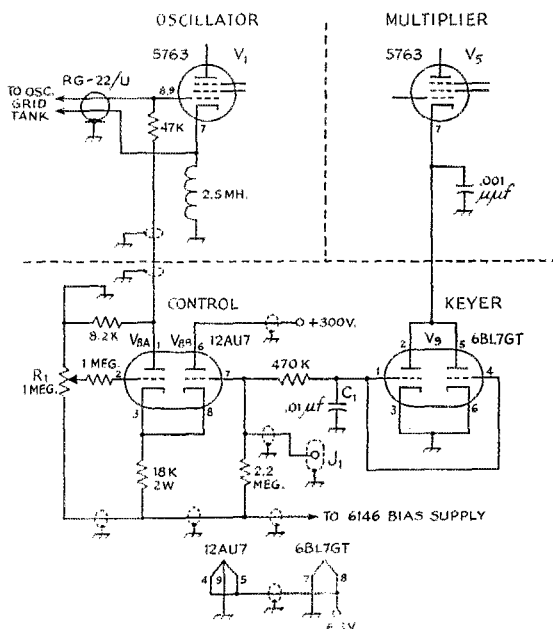


Fig. 5 — Circuit diagram of the differential keyer as connected to the 813 transmitter. Oscillator and multiplier wiring not shown is identical to that of the original transmitter. Capacitors are disk or tubular ceramic. All resistors  $\frac{1}{2}$  watt unless otherwise specified.  $J_1$  is the original key jack for the transmitter and  $R_1$  is a 1-megohm potentiometer.

<sup>4</sup> Puckett, "De Luxe Keying without Relays." *QST*, September, 1953.

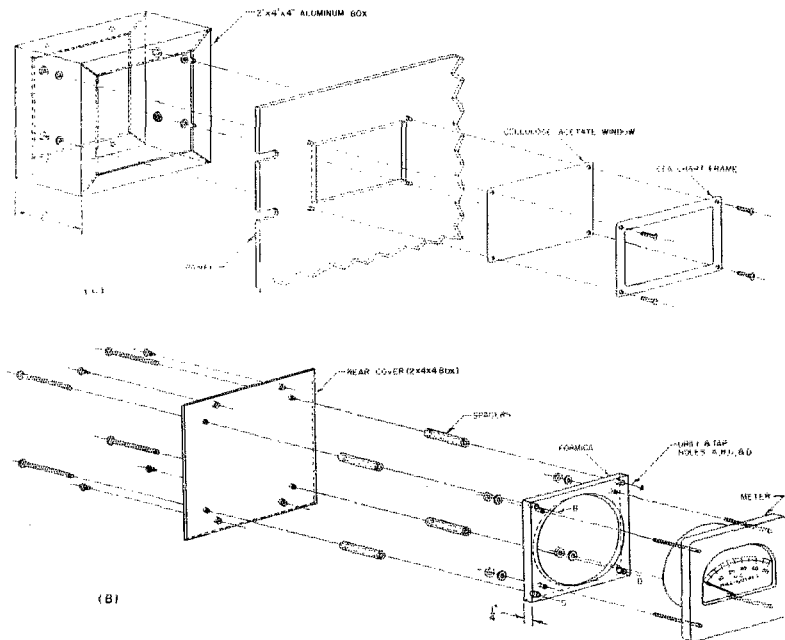


Fig. 6 — The chart frame, the panel and the aluminum box are held together, as shown in A, by the hardware supplied with the CFA. B shows a meter (Triplett Model 327-T), its insulated mounting ring, and the rear cover of the box. The meter assembly is slipped into the metal box after the latter has been attached to the rear of the panel. Shielded meter leads enter the bottom of the box through a rubber grommet. The shield braid should be bonded to the outside of the aluminum case at the point of entry.

The 100-ohm shunt in the screen lead to the 813 has been replaced with a 1-ohm, 1-watt resistor. This increases the full-scale reading of the 50-ma. meter to 100 ma. and prevents pinning of the pointer by high screen current drawn during tuning adjustments.

The parallel-tuned circuit formed by  $C_7$ ,  $C_{11}$  and  $RFC_3$  (approximately 250  $\mu\text{f.}$  in parallel with 2  $\mu\text{h.}$ ) has a natural resonance somewhere around 7 Mc. which may cause heating of the choke, harmonic output, or TVI difficulties. A check with a grid-dip meter will let you know if the resonant frequency needs moving. Raising or lowering the value of any one of the three components involved will do the trick.

Although we don't particularly recommend it, crystal control can be added to the transmitter provided you are prepared for some rather difficult mechanical problems. The oscillator revision may be patterned after the circuitry used in the remotely-tuned v.f.o. described elsewhere.<sup>6</sup> However, a great deal of care went into the mechanical design of the v.f.o. for the 813 rig, and it is difficult to visualize any switching or plug-in arrangement permitting crystal-v.f.o. operation that will not affect the stability of the v.f.o.

#### General Information — Mechanical

Procurement of a National type ACD-1 right-angle drive has been impossible for many con-

structors. Production of the unit was stopped shortly after the transmitter was completed. However, the National type RAD drive, now available, fits the application very nicely.

The meter boxes were improperly identified in *QST* for June, 1954. They are ICA type 29840 — not type 29804 as listed.

A new sketch of the mounting and the shielding of the meters is presented herewith as Fig. 6. Section A of the drawing shows the assembly formed by the chart frame and its cellulose-acetate window, the panel and an aluminum box. The front cover for the box is not used.

Section B of Fig. 6 shows the support for a meter. The distance from the face of the meter to the rear cover should not exceed  $1\frac{1}{8}$  inches. Reduce the length of the threaded meter terminals if necessary.

WISTX has just informed us that the full-scale drilling template for the transmitter is still available. See the Ham-ad on page 147, *QST*, July, 1955, for further information.

We are able to furnish 8  $\times$  10-inch glossy prints of any or all of the photographs illustrating the articles (including the shots shown in this issue), at \$1.00 per print, postpaid.

As is Headquarters' policy, each future inquiry about the transmitter will receive individual attention. However, we believe that the preceding articles<sup>1,2</sup> and this current write-up present just about every bit of constructional and operational data that there is to offer.

<sup>6</sup> Mix, "Simple Remote Tuning for the V.F.O.," *QST*, January, 1953. Also *The Radio Amateur's Handbook*, 31st-33rd editions.